

**ELECTRICAL TECHNOLOGY: ELECTRONICS**

**EXAMINATION NUMBER**


--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**ANSWER SHEET**


**Attach this Answer Sheet as the last page to your Answer Book.**

**Complete your sketches in pen.**

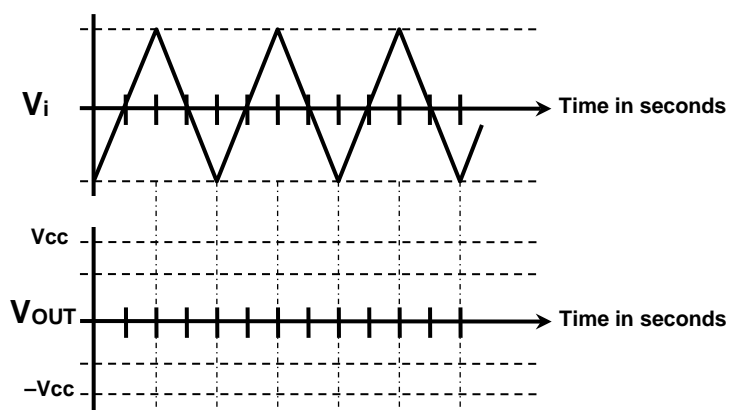
**QUESTION 5.5.2 SWITCHING AND CONTROL CIRCUITS**



(2)

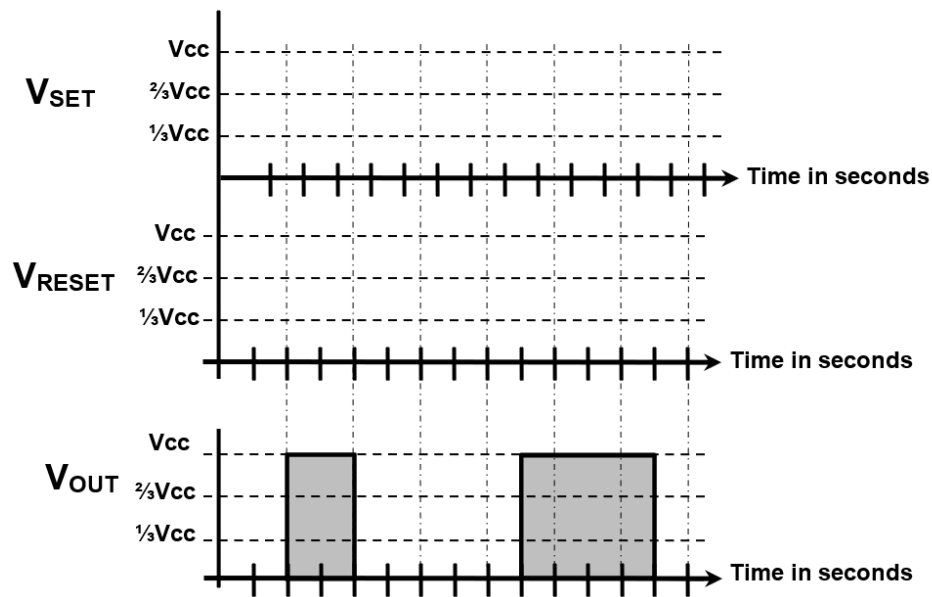**QUESTION 5.7.2**

(5)

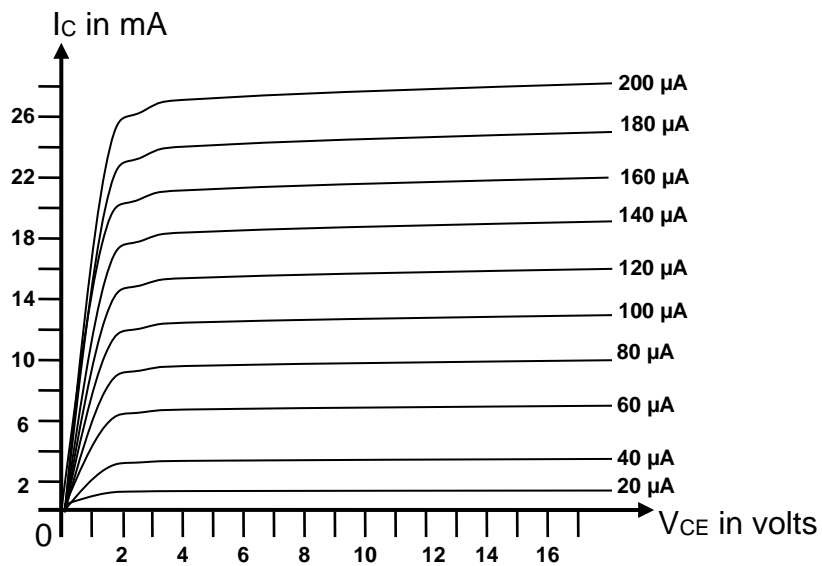**QUESTION 6.1.4 AMPLIFIERS**

(3)